

# Lecture 12

## Counters & Shift Registers

---



# Outline

- Counters (\*\*)
- Shift Registers (\*\*)
- Textbook Chapter 11.1 and 11.2



# Counters-Overview

- Special sequential circuits (Finite State Machine) that sequence through a set of outputs.
- Examples:
  - binary counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, 001, ...
  - gray code counter: 000, 010, 110, 100, 101, 111, 011, 001, 000, 010, 110, ...
  - one-hot counter: 0001, 0010, 0100, 1000, 0001, 0010, ...
  - BCD counter: 0000, 0001, 0010, ..., 1001, 0000, 0001
  - pseudo-random sequence generators: 10, 01, 00, 11, 10, 01, 00, ...



# Counter in General


- In general: counters simplify controller design by
  - providing a specific number of cycles of action
  - sometimes used with a decoder to generate a sequence of control signals
- It is a special case of Finite State Machine (FSM)
- Can be asynchronous or synchronous
  - Synchronous counter is always preferred
    - Easier to implement in RTL



# Ripple Counter: Asynchronous


A3	A2	A1	A0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

time

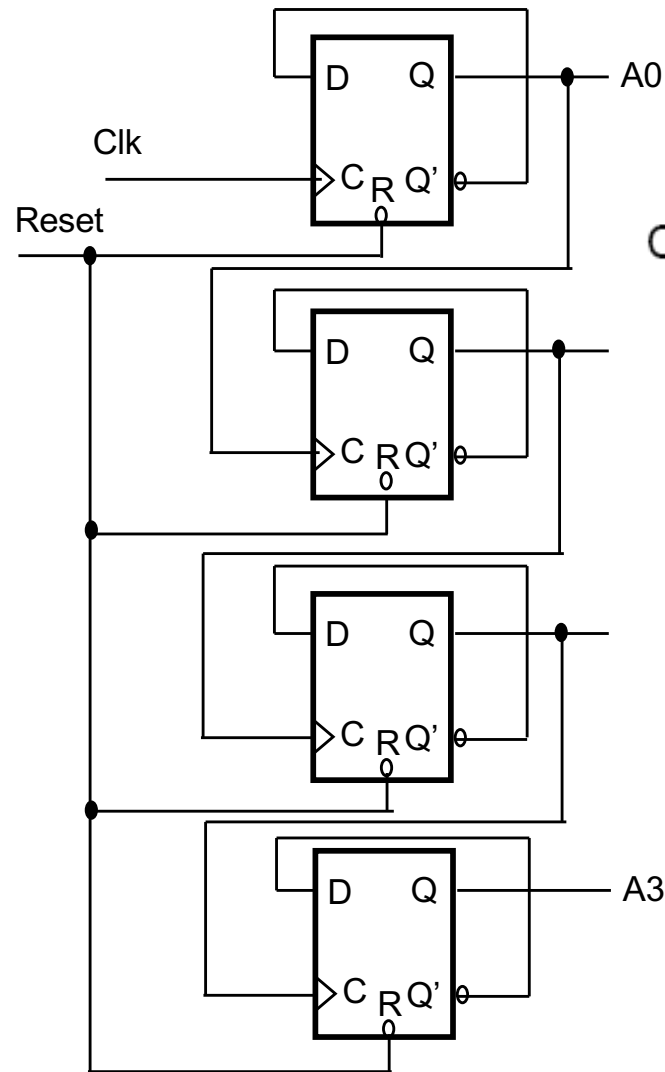

Each stage is  $\div 2$  of previous

- Look at output waveforms:

 

Since clock inputs of some FFs are actually not driven by the clock, ripple counters are called asynchronous counters



# Synchronous Counters


- *All outputs change with clock edge*
- Binary Counter Design: Start with 3-bit version and generalize:

c	b	a	c+	b+	a+
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$$a^+ = a'$$

$$b^+ = a \text{ XOR } b$$

		cb			
a	00	01	11	10	
	0	0	1	1	
	0	0	1	1	
	1	0	1	0	

 

$$c^+ = a'c + abc' + b'c$$

$$= c(a' + b') + c'(ab)$$


$$= c(ab)' + c'(ab)$$

$$= c \oplus ab$$


 
# Synchronous Counters

- How do we extend to n-bits?
- Extrapolate  $c^+$ :  $d^+ = d \text{ xor } abc$ ,  $e^+ = e \text{ xor } abcd$




Cons: Has difficulty scaling (AND gate inputs grow with  $n$ )



# Synchronous Counters

- How to stop earlier?
- Extra logic can be added to stop counting before reaching the maximum
  - Example: count to 11

set counts  
back to 0

 





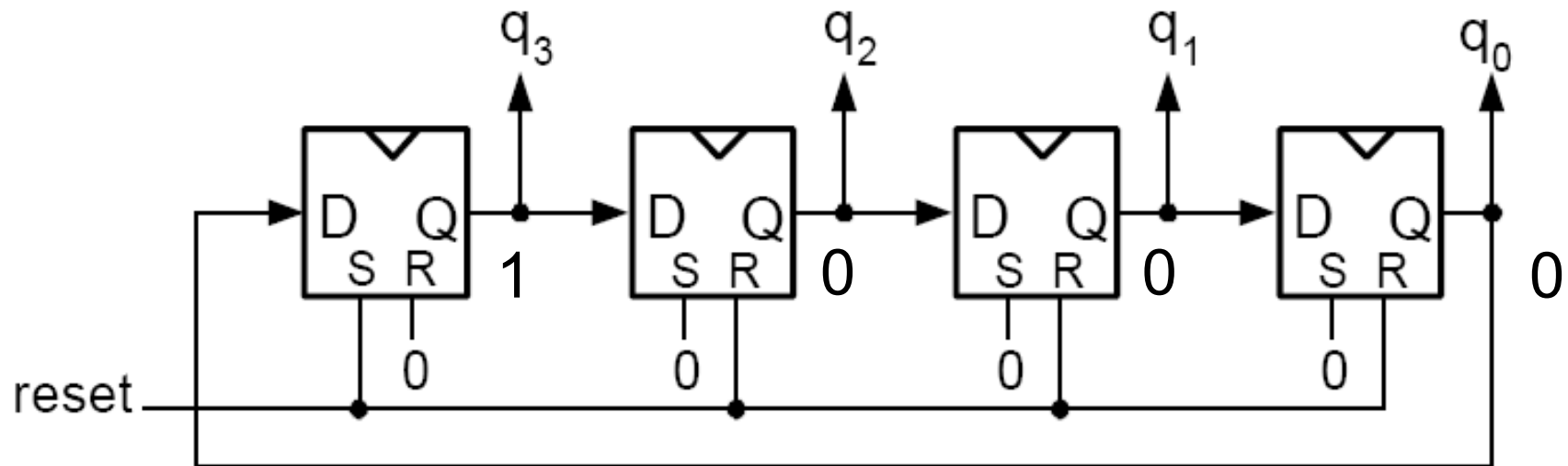
# Ring Counters


- “one-hot” counters  
0001, 0010, 0100, 1000, 0001, ...





# Ring Counters

- Counter with a decoder at its output

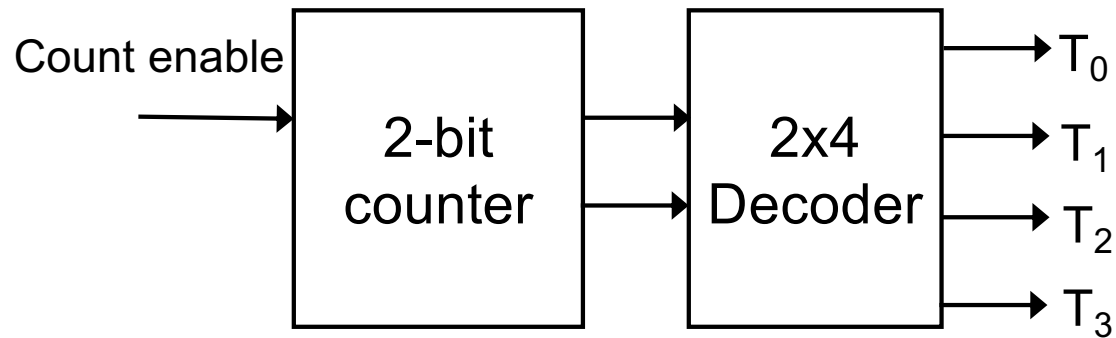




# Example of Verilog Code: Counter

```
module counter (in, clk, rstb, out);  
    input in, clk, rstb;  
    output [3:0] out;  
    reg [3:0] out;  
    always @ (posedge clk or negedge rstb)  
        if (rstb == 1'b0) begin  
            out <= 4'b0000;  
        end  
        else if (out == 4'b1111 && in == 1'b1) begin  
            out <= 4'b0000;  
        end  
        else if (in == 1'b1) begin  
            out <= out + 1;  
        end  
end  
endmodule
```


 
# Registers-Summary


- Based on flip flops: store internal values or states





# Registers


- Load Enable: load new data when load=1

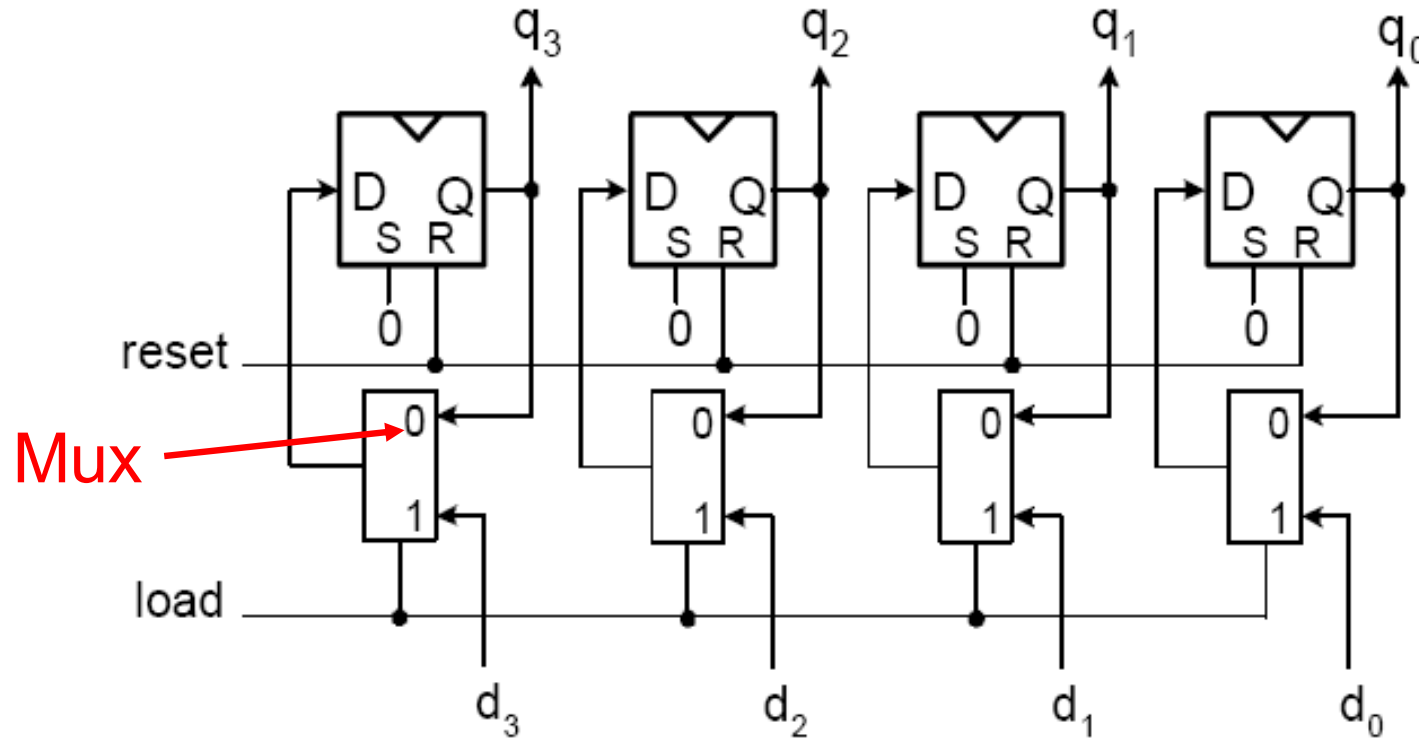



# Shift Registers


- Parallel Load Shift Register

 

- “Parallel-to-serial converter”: parallel load data
- After loading data, shift bits by bits
- Commonly used in low speed IO, e.g. scan chains



# Universal Shift Register

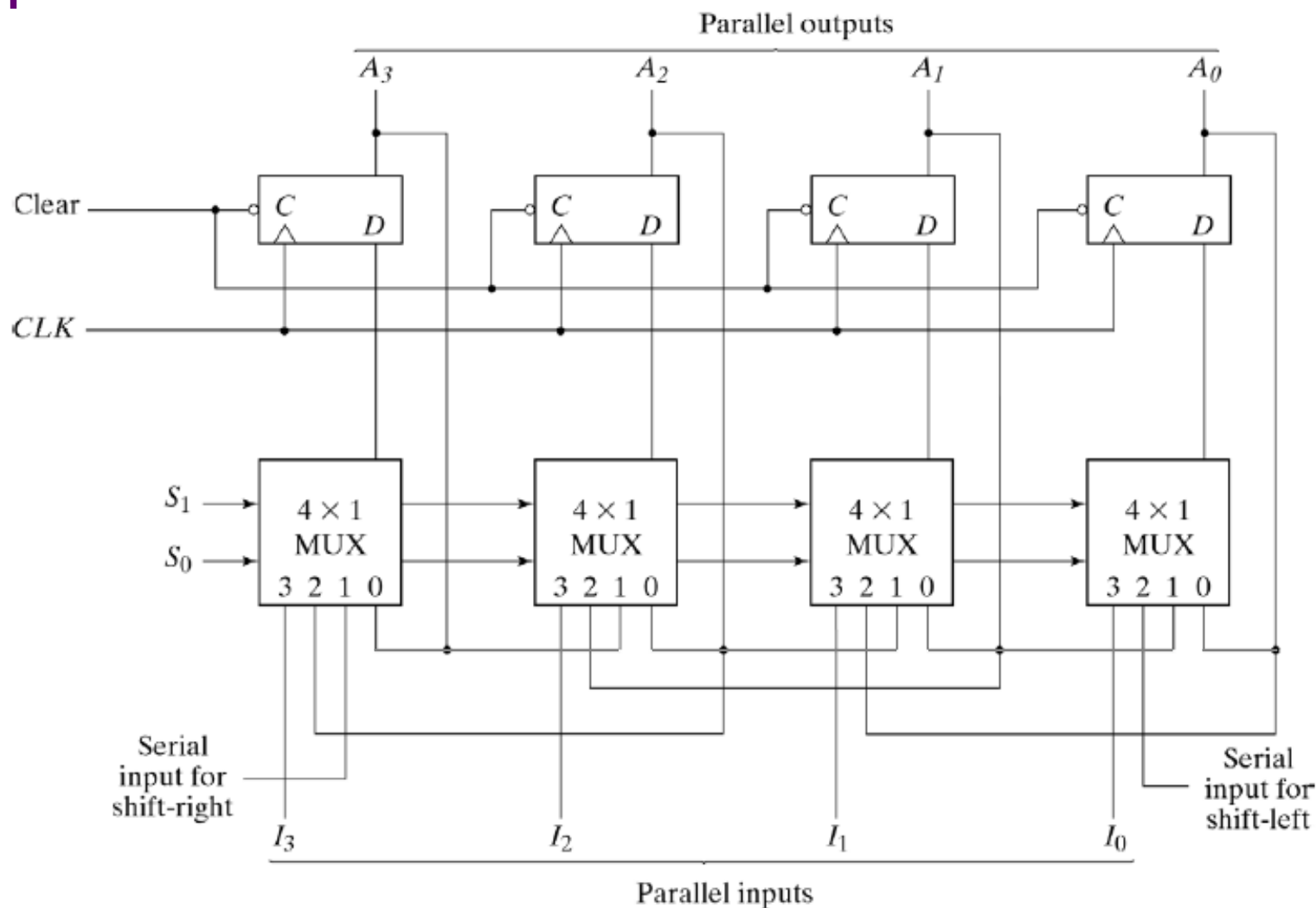

$S_1$  and  $S_0$ :  
00: Retention  
01: shift-right  
10: shift-left  
11: parallel load



# Example of Verilog: Universal Shift Register

```
module Shift_Register( CLK,CLR,RIN,LIN,S0,S1,A,B,C,D,QA,QB,QC,QD );
  input CLK, CLR, S0, S1, RIN, LIN, A, B, C, D;
  output reg QA, QB, QC, QD;
  always @ (posedge CLK) begin
    if (CLR == 1'b1) {QA,QB,QC,QD} <= 4'b0;
    else case ({S1,S0})
      2'b00: ; // Hold
      2'b01: {QA,QB,QC,QD} <= {RIN,QA,QB,QC}; // Shift right
      2'b10: {QA,QB,QC,QD} <= {QB,QC,QD,LIN}; // Shift left
      2'b11: {QA,QB,QC,QD} <= {A,B,C,D}; // Load
      default: {QA,QB,QC,QD} <= 4'bx; // shouldn't occur
    endcase
  end
endmodule
```





# Appendix