

Lecture 10

Finite State Machine



Outline

- Basics of Finite State Machine (***)
- State Reduction (***)
- Textbook chapters: 9.1-9.4



Building Finite State Machines

- We will first review an example



Example: Sequence Detector

**Assert output whenever a sequence of [1 0] is detected in the input stream
Otherwise output is 0**

Input 1 0 0 1 1 0 1 0 1 1 1 0

Output 0 1 0 0 0 1 0 1 0 0 0 1




Process for creating a circuit for FSM

 - 1. Analyze the verbal problem statement*
- 2. Create example input/output sequences that represent typical scenarios*
- 3. Going through these sequences,*
 - a. Either create a new state and branch out for the corresponding input case*
 - b. Revisit an existing state that covers this input behavior*
- 4. For each state, transitions for all possible input combinations must be accounted for*
- 5. For each possible transition, the output response must be attached*



Process for creating a circuit for FSM

- Always start with the 'initial'/'reset' state
 - How will the circuit react for all input cases starting at this state?






Process for creating a circuit for FSM

- How will the circuit react for all input cases starting at this state
 - If input is '0' that will be the case of the FSM 'having spotted a 0': a new state S2
 - If input is '1' that will be the case of the FSM having spotted a 1': different that spotting a '0', a new state S3
 - In both of these new states output is still '0' no '10' pattern detected

 
Circle = output response
Branches = input





Process for creating a circuit for FSM

- Cover all outgoing transitions from each new state added
 - @S2:
 - If input is '0' the status of the FSM is no different, self loop back to S2
 - If input is '1' that is the first '1' spotted yet, which is the same situation as being in S3, transition to S3
 - @S3:
 - If input is '0' that is a '10' pattern DETECTED, this is a new event, NEW State S4, with output of new state = '1'
 - If input is '1' the status of the FSM is no different, self loop back to S3

 




Process for creating a circuit for FSM

- Cover all outgoing transitions from each new state added
 - @S4:
 - If input is '0', this is no different than having seen 'just any sequence' 0s, transition to S2
 - If input is '1', this is no different than having seen 'just any sequence' 1s, transition to S3

 State 1: this is a safe way to do initialization





Finite State Machine Basics

- State updated at rising edge of clock
- With n bits, we can realize 2^n states in total
- Two types of FSM: Mealy or Moore State Machine

Mealy Machine:

Next state = $F(\text{current state}, \text{input})$

Output = $G(\text{current state}, \text{input})$


Moore Machine:

Next state = $F(\text{current state}, \text{input})$

Output = $G(\text{current state})$



Moore versus Mealy machines

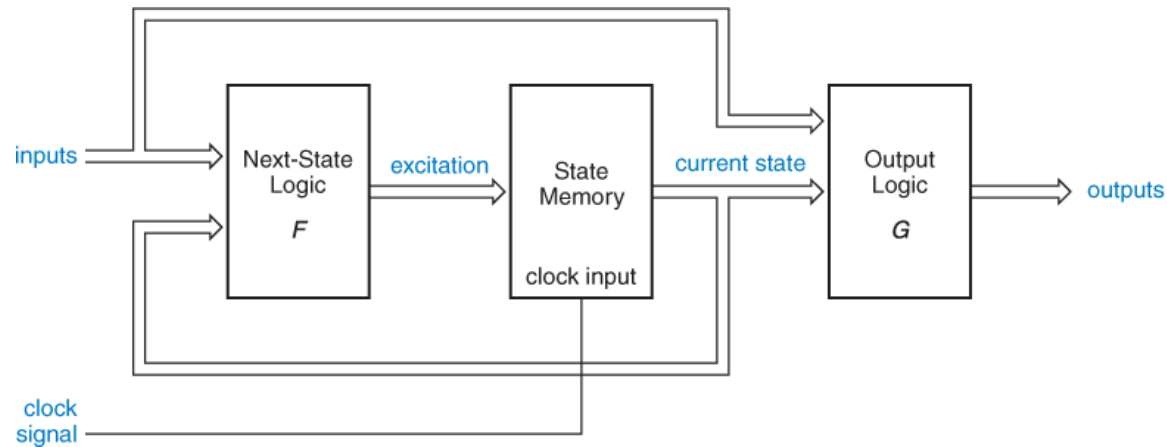

Mealy machine

Outputs depend on state
and on inputs


Input changes can cause
immediate output changes
(asynchronous)

Not necessarily follow the clock

Moore machine

Outputs are a function
of current state

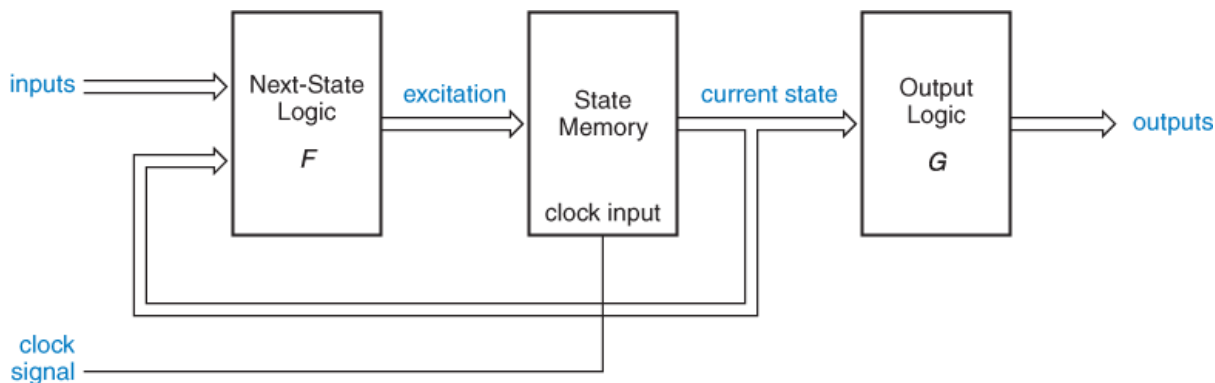
Outputs change
synchronously with
state changes



Let 9 last example is a Moore machine - the result does not explicitly depend on the inputs



Timing Diagram of FSM

 

- Note that the outputs of Moore's machine are synchronous while Mealy's are not




Comparing Moore and Mealy machines

- Mealy state machines
 - + Typically have fewer states
 - + React faster to inputs — don't wait for clock
 - Asynchronous outputs can be dangerous
- Moore state machines
 - + Safer to use because outputs change at clock edge
 - May take additional logic to decode state into outputs
- Alternatively, design synchronous Mealy machines
 - Design a Mealy machine
 - Then register the outputs



Mealy Machine with Pipelined Outputs

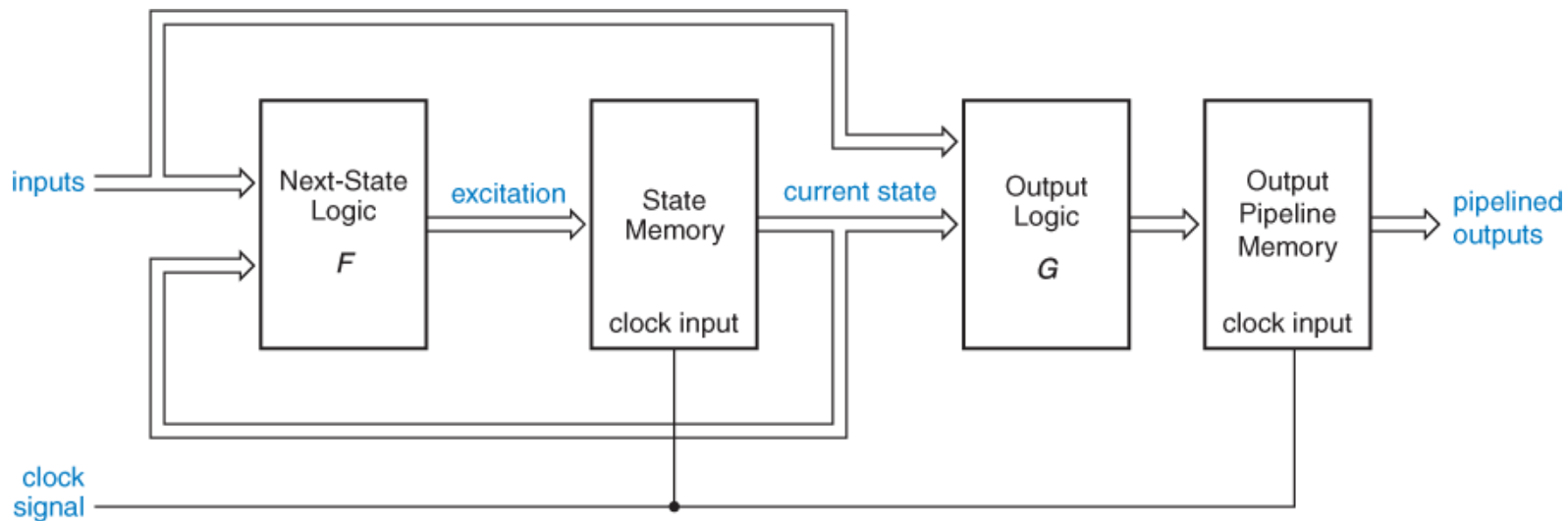
- Registered state **and registered outputs**
 - No glitches on outputs
 - No race conditions between communicating machines






State Diagram

MAX/MAXS is output

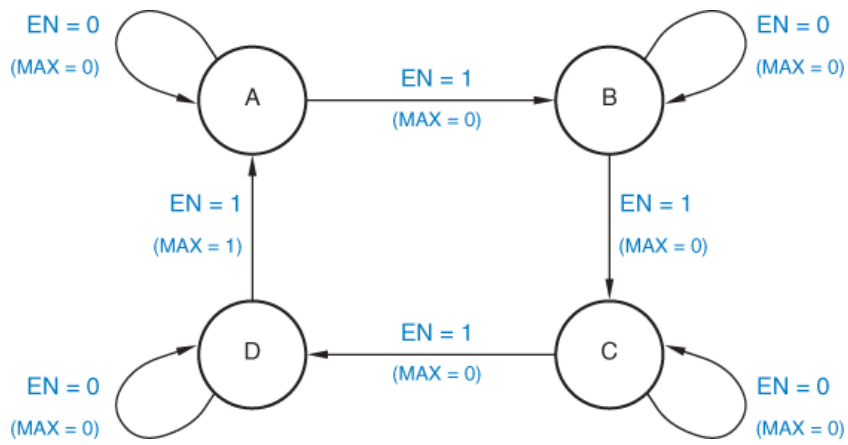

Mealy Machine

 

Moore Machine

- Use graphical format to represent state transition table



FSM Example

This table tells that this is a Mealy machine

Transition Table

Q1Q0	Q1*Q0*	
Q1Q0	EN=0	EN=1
00	00	01
01	01	10
10	10	11
11	11	00

State Table

S	S*	
	EN=0	EN=1
A	A	B
B	B	C
C	C	D
D	D	A

State/Output Table


S	S*, MAX	
	EN=0	EN=1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1

- Use tables to represent transition relationships
- Can use alphanumeric state names , e.g. A, B, S0, S1 to replace "00", "01" etc.



FSM Example

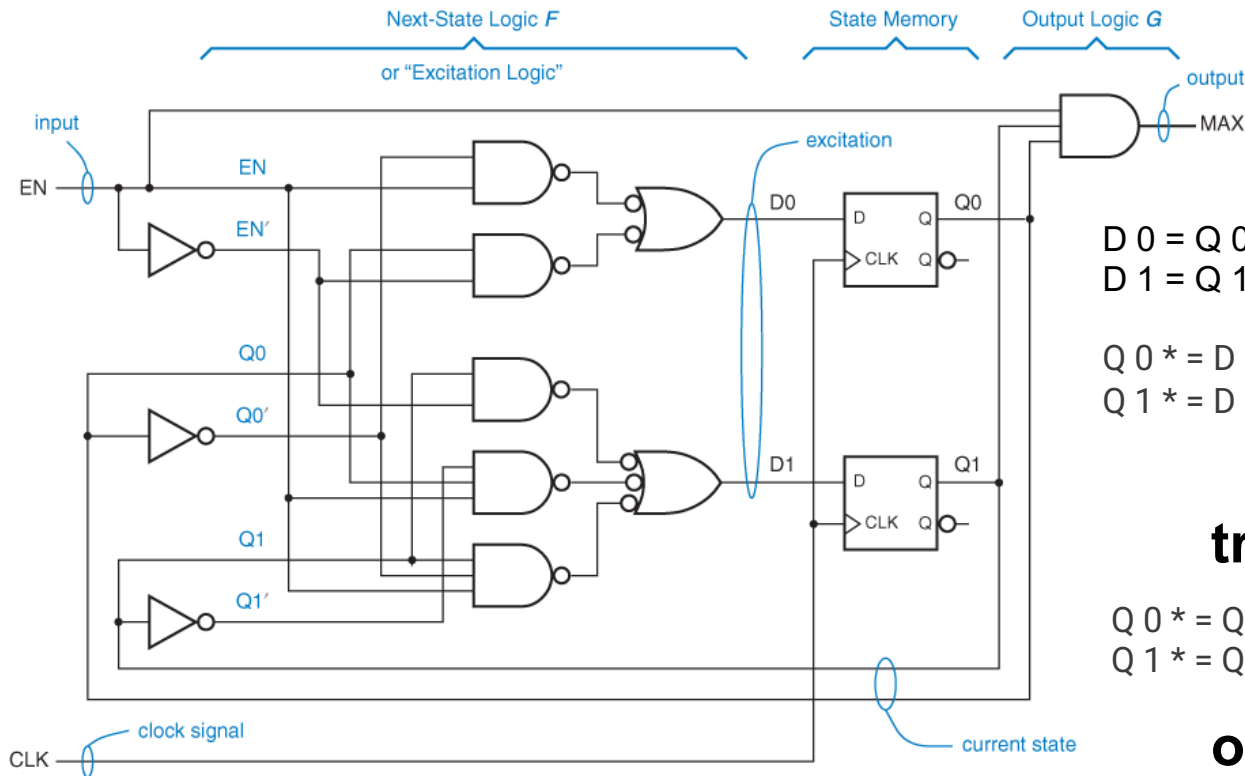We provide FSM, genius generate the circuits



$$D0 = Q0 \cdot EN' + Q0' \cdot EN$$

$$D1 = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

$$Q0^* = D0$$

$$Q1^* = D1$$



transition equation

$$Q0^* = Q0 \cdot EN' + Q0' \cdot EN$$

$$Q1^* = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

output equation

$$MAX = Q1 \cdot Q0 \cdot EN$$

- Circuits are built to realize transition table/equations




State Minimization

Implement FSM with fewest possible states

- Least number of flip-flops
Number of distinct states to be encoded correlates with the number of flip flops that will store the codes for those states
- Boundaries are power of two number of states
- Reduce the number of gates needed for implementation of the combinational logic that fires up the state code contents of the memory elements




State Reduction

 

	Next state		
Present State	I = 0	I = 1	Output
A	A	B	0
B	C	B	0
C	A	B	0
D	A	A	1



State Reduction

 


**Same next state
for same input
AND same output**

	Next state		
Present State	I = 0	I = 1	Output
A	A	B	0
B	C	B	0
C	A	B	0
D	A	A	1



State Reduction

 

	Next state		
Present State	I = 0	I = 1	Output
AC	AC	B	0
B	AC	B	0
D	AC	AC	1


A and C are equivalent

Give a common new name (AC) and let one of them also represent both (remove one state from the table)

Update all states named A or C as AC



State Reduction

 

	Next state		
Present State	I = 0	I = 1	Output
ABC	ABC	ABC	0
D	ABC	ABC	1

AC and B are equivalent

Give a common new name (ABC) and let one of them also represent both (remove one state from the table)

Update all states named AC or B as ABC



State Reduction

Identify and combine states that have equivalent behavior

Equivalent States: for all input combinations, states transition to the same or equivalent states, as well as same output behavior



State Reduction

Algorithmic Approach!!!

- Start with state transition table
- Identify states with same output behavior
- If such states transition to the same next state, they are equivalent
- Combine into a single new renamed state
- Repeat until no new states are combined

But How??



Systematic Approach to State Reduction

- Sometimes equivalency is not so obvious
- Implication Chart



Implication Chart

Current state	Next state		output
	I=0	I=1	
A	B	E	0
B	C	D	0
C	D	D	0
D	A	A	1
E	D	D	0

It is not obvious whether A and B are equivalent

If A and B were to be equivalent, then

B and C have to be equivalent

E and D have to be equivalent

In this case, we see that E and D are not (their output behavior does not match), hence this implies that A and B cannot be equivalent



Implication Chart

1. Construct implication chart, one square for each combination of states taken two at a time


B				
C				
D				
E				
	A	B	C	D



Implication Chart

1. Construct implication chart, one square for each combination of states taken two at a time
2. Square labeled (S_i, S_j) Enter in each box the implication of the equivalence (comparing $I=0$ and
 - if outputs differ than square gets X If output mismatch, then imply they cannot be
 - Otherwise write down implied state pairs for all input combinations
 - If the equivalency is directly observable the square gets 1

B	B=C D=E			
C	B=D D=E	C=D		
D	X	X	X	
E	B=D D=E	C=D	1	X
	A	B	C	D

 

	Next state		
Current state	I=0	I=1	output
A	B	E	0
B	C	D	0
C	D	D	0
D	A	A	1
E	D	D	0



Implication Chart

2. Square labeled (S_i, S_j)
 - if outputs differ then square gets X
 - Otherwise write down implied state pairs for all input combinations
 - If the equivalency is directly observable the square gets 1
3. Advance through chart top-to-bottom and left-to-right
 - If square (S_i, S_j) contains next state pair S_m, S_n and that pair has a square already labeled X , then S_i, S_j is also labeled X

B	B=C D=E			
C	B=D D=E	C=D		
D	X	X	X	
E	B=D D=E	C=D	1	X
	A	B	C	D



B	X			
C	X	C=D		
D	X	X	X	
E	X	C=D	1	X
	A	B	C	D



Implication Chart

2. Square labeled (S_i, S_j)
 - if outputs differ than square gets X
 - Otherwise write down implied state pairs for all input combinations
 - If the equivalency is directly observable the square gets 1
3. Advance through chart top-to-bottom and left-to-right
 - If square (S_i, S_j) contains next state pair S_m, S_n and that pair has a square already labeled X , then S_i, S_j is also labeled X

B	X			
C	X	C=D		
D	X	X	X	
E	X	C=D	1	X
	A	B	C	D



B	X			
C	X	X		
D	X	X	X	
E	X	X	1	X
	A	B	C	D



Implication Chart

2. Square labeled (S_i, S_j)
 - if outputs differ than square gets X
 - Otherwise write down implied state pairs for all input combinations
 - If the equivalency is directly observable the square gets 1
3. Advance through chart top-to-bottom and left-to-right
 - If square (S_i, S_j) contains next state pair S_m, S_n and that pair has a square already labeled X , then S_i, S_j is also labeled X
4. Continue executing Step 3 until no new squares are marked with X
5. For each remaining unmarked square S_i, S_j , then conclude S_i and S_j are equivalent

B	X			
C	X	X		
D	X	X	X	
E	X	X	1	X
	A	B	C	D

C and E are the only equivalent pair




Implication Chart-Summary

1. Construct implication chart, one square for each combination of states taken two at a time
2. Square labeled (S_i, S_j)
 - if outputs differ than square gets X
 - Otherwise write down implied state pairs for all input combinations
3. Advance through chart top-to-bottom and left-to-right
 - If square (S_i, S_j) contains next state pair S_m, S_n and that pair has a square already labeled X , then S_i, S_j is also labeled X
4. Continue executing Step 3 until no new squares are marked with X
5. For each remaining unmarked square S_i, S_j , then conclude S_i and S_j are equivalent



Multiple Input State Diagram Example

 


State Diagram

Present State	Next State				Output
	00	01	10	11	
S ₀	S ₀	S ₁	S ₂	S ₃	1
S ₁	S ₀	S ₃	S ₁	S ₅	0
S ₂	S ₁	S ₃	S ₂	S ₄	1
S ₃	S ₁	S ₀	S ₄	S ₅	0
S ₄	S ₀	S ₁	S ₂	S ₅	1
S ₅	S ₁	S ₄	S ₀	S ₅	0

Symbolic State Diagram



Example (contd)

 

Present State	Next State				Output
	00	01	10	11	
S ₀	S ₀	S ₁	S ₂	S ₃	1
S ₁	S ₀	S ₃	S ₁	S ₅	0
S ₂	S ₁	S ₃	S ₂	S ₄	1
S ₃	S ₁	S ₀	S ₄	S ₅	0
S ₄	S ₀	S ₁	S ₂	S ₅	1
S ₅	S ₁	S ₄	S ₀	S ₅	0

Minimized State Table

**S3 and S5
S0 and S4
are equivalent**



Hemmi

Appendix