

# Lecture 6

## Verilog Language 2

---

# Outline

- Verilog Language
  - Examples of three Verilog styles
  - Procedure Statement
  - Simulation



# Important Verilog Constructs

- Gate-level primitives
  - Built-in
  - User defined
- Module Instantiation Statement
  - Used in Structural Style code Structural style example: `and g1(e, a, b)`
- ASSIGN Statement Example: `assign x = e ^y`
  - Concurrent signal assignment Concurrent = happen at the same time (combinational)
  - Used in both In both structural and gate-level
- INITIAL Statement (Block)
  - Used in Behavioral Style – for simulation purposes
- ALWAYS Statement (Block)
  - Used in Behavioral Style



# Built-in Gate Level Primitives

- The following are provided as built-in:

and	nand	logical AND/NAND
or	nor	logical OR/NOR
xor	xnor	logical XOR/XNOR
buf	not	buffer/inverter
Bufif0	notif0	Tristate with low enable
bifif1	notif1	Tristate with high enable

Tristate buffers are allowed to connect to one single wire  
Buffer require a control enabled signal



# User Defined Primitive

```
Primitive my_own_gate(out, a, b, c);  
output out;  
input a, b, c;  
table  
  00? : 1;  
  000 : 0;  
  ?00 : 0;  
  11? : 1;  
  1?1 : 1;  
  ?11 : 1;  
endtable  
endprimitive
```

? : Don't Care




# Module Instantiation for Structural Models

- Structural models
  - Are built from gate primitives and/or other modules
  - They describe the circuit using logic gates — much as you would see in an implementation of a circuit.
- Identify
  - Gate instances, wire names





# Module Instantiation Using Primitives

 

```
module mux (f, a, b, sel);  
    output    f;  
    input     a, b, sel;  
  
    wire      f1, f2, nsel;  
    and       g1 (f1, a, nsel),  
           g2 (f2, b, sel);  
    or        g3 (f, f1, f2);  
    not       g4 (nsel, sel);  
endmodule
```



# Module Instantiation Using Other Modules Previously Defined

- There is a Flip Flop module with clock, data, q, qBar, reset, preset ports:
- Note the explicit matching of ports. Some ports can be left unused.
- Implicit listing of connections is also allowed, following the convention of position:

- **d\_ff d\_ff\_instance1(clk, d[0],q[0], , , );**  
**//qBar, reset, and preset ports are left unused**

```
module d_ff_two(clk,d,q);  
    input clk;  
    input [1:0] d;  
    output [1:0] q;  
    d_ff d_ff_instance1(.clk (clk), .d (d[0]), .q (q[0]));  
    d_ff d_ff_instance2(.clk (clk), .d (d[1]), .q (q[1]));  
  
endmodule
```





# ASSIGN (Concurrent) Statement

- Operation happens concurrently, ordering does not matter;
- Used for combinational logic
  - Structural Primitive/Module Instantiations could also be considered as a type of concurrent statement
- Continuous assignments: used in RTL design

`assign e=A & B;`



# Continuous Assignment

```
wire [8:0] sum;
```

```
wire [7:0] a, b; ← Define bus widths
```

```
wire carryin;
```

```
assign sum = a + b + carryin;
```

Continuous  
assignment:  
permanently sets the  
value of sum to be  
 $a+b+carryin$   
Recomputed when a, b,  
or carryin changes



# Describing Combinational Logic

```
module mux21 (mux_out, in1, in2, sel)
input in1, in2, sel;
output mux_out;

assign mux_out = (sel==0) ? in0: in1;

endmodule
```

```
module some_logic (d1_out, d2_out, in1, in2)
input [3:0] in1, in2;
output [3:0] d1_out, d2_out;

assign d1_out = in1 & in2;
assign d2_out = ~in1 | in2;

endmodule
```



# Procedural Statement

- Procedural Statements
  - Used to describe sequential circuits
  - Define “Sequential operation”, order matters
- Two main code structures
  - Initial Block
  - Always Block



# Initial and Always Blocks

- Basic components for behavioral modeling

**initial**

**begin**

**... imperative statements**

**...**

**end**

**Runs when simulation starts**

**Terminates when control  
reaches the end**

**Good for providing stimulus**

**always**

**begin**

**... imperative statements**

**...**

**end**

**Runs when simulation starts**

**Restarts when control  
reaches the end**

**Good for  
modeling/specifying  
hardware**



# Initial Statement

- Inserted into code to support simulation
  - Use it to define a sequence of operations to set up the initial conditions of signals
- By default executed once **when simulation starts**
- **Terminates when last statement in the block is reached**
- Not synthesizable
- Can also use multiple initial statements for events operating in parallel



# Initial Examples

```
module clk_gen();
```

```
reg clk, reset;
```

```
initial begin
```

```
    clk = 0;
```

```
    reset = 0;
```

```
    #2 reset = 1;
```

```
    #5 reset = 0;
```

```
End
```

```
always
```

```
begin
```

```
    #1 clk = !clk;
```

```
end
```

```
module stimulus_gen;
```

```
reg a, b;
```

```
initial begin
```

```
    a = 0;
```

```
    b = 0;
```

```
    #5 a = 1;
```


```
    #5 b = 1;
```

```
    #5 a = 0;
```

```
    #5 b = 0;
```

```
end
```

```
endmodule
```

 



# Always Statement

- One of the most important constructs in Verilog to describe behavior
- Two main places to use
  - Define an iterative sequential event
    - Used in a testbench
  - Define sequential circuits, e.g. flip-flops
- Can also describe combinational logic, if used carefully in limited context





# Always for Generating Repetitive Events

```
module testbench ()
```

```
initial begin
```

```
    clk= 0;
```

```
    d = 0;
```

```
end
```

```
always begin
```

```
    #5 clk= ~clk;
```


```
end
```

```
always begin
```


```
    #10 d = ~d;
```

```
end
```


```
endmodule
```

 


Only execute once

 

 Uses a **Delay Statement** - **#5** - to control timing of when the always block will restart



 Executes every 5ns  
(Creates a clock with  
10ns period)



Executes every 10ns



# Always for Sequential Logic

- Sequential logic only updates values upon clock transition
  - Described using the sensitivity list feature of the always statement
  - always statement restarts upon the described event statement in the sensitivity list

Three main ways to list:

`always @(posedge clk) //special construct for sequential circuits`

`always @(signal1, signal2) //explicit list of signals`


`always @(*) Wildcard`



# Always for Sequential Logic
 
## Simple flip-flop behavior

```
module dff(D, clk, Q);  
    input D, clk;  
    output reg Q;  
    always @(posedge clk)  
        Q = D;  
endmodule
```





# Always for combinational logic


```
always @(A, B) begin
```

```
    C = A & B;
```

```
end
```

Sensitivity list

List all signals you want to be involved

 

AND gate




# Always for combinational logic

```
always @(*) begin
```

```
    C = A & B;
```

```
end
```

 

AND gate

Sensitivity list  
Wildcard Statement \*  
Compiler identifies all  
Signals that are “read”



# Procedural Assignment

- Inside an initial or always block:

`sum = a + b + cin;`

- Similar to the **assign** statement, but functions within the sequential execution context
- RHS evaluated and assigned to LHS before next statement executes
- RHS may contain wires and regs
  - Two possible sources for data
- LHS must be a reg



# Blocking vs. Non-blocking Assignments

- Verilog has two types of procedural assignments:

Blocking Assignment – Non-Blocking Assignment

`C = A & B; //Simple blocking assignment`  
`// C updated immediately`

`C = #Time A & B; //Blocking assignment with delay`  
`//Execution halted for "Time" and then C updated`



# Blocking vs. Non-blocking Assignments

- Fundamental problem:
  - In a synchronous sequential circuit, all flip-flops sample simultaneously as they wake up with the clock tick
  - Assignment inside the always @(posedge clk) block run in some undefined sequence





# Blocking vs. Non-blocking Assignments

- Non-Blocking Assignment

always @(posedge clk)

```
C <= A & B; //Non-blocking assignment
```

```
D <= !C;
```

```
// Right Hand Side will be evaluated, but the value of C will not be  
// updated. Execution will move onto the next statement (it will use  
// C's old value) C is updated before the next activation on the  
// always block (i.e., by next clock tick)
```



# Interaction Among Blocking Statements

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 = d1;  
always @(posedge clk) d3 = d2;  
always @(posedge clk) d4 = d3;
```

//These run in some order, but it  
// is not deterministic  
//will d3 take on d2's old value of  
// its new value as updated by d1?

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk)  
d1= ext_in;  
d2 = d1;  
d3 = d2;  
d4 = d3;
```

//all registers contain same  
// value (ext\_in) each clock tick



# Interaction among Non-Blocking Statements

- A sequence of non-blocking assignments do not communicate

a = 1;  
b = a;  
c = b;

Blocking assignments:  
a = b = c = 1

a <= 1;  
b <= a;  
c <= b;

Non-blocking assignments:  
a = 1  
b = old value of a  
c = old value of b



# Non-blocking Assignments

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d1 <= ext_in;
```

```
always @(posedge clk) d2 <= d1;
```

```
always @(posedge clk) d3 <= d2;
```

```
always @(posedge clk) d4 <= d3;
```


Nonblocking rule:  
RHS evaluated  
when assignment  
runs

LHS updated only after all  
events for the current  
instant have run




# Blocking looks like chain of wires, Non-blocking Looks Like Chain of Registers

```
a = 1;  
b = a;  
c = b;
```

 

```
a <= 1;  
b <= a;  
c <= b;
```

 



# Imperative Statements:

## If Statement

## Case Statement

```
if (select == 1)
    y = a;
else
    y = b;
```


```
case (op)
    2' b00: y = a + b;
    2' b01: y = a - b;
    2' b10: y = a ^ b;
    default: y = 'hxxxx;
endcase
```



# Always for Sequential Logic with If Statement
 
## Flip Flop with Negative Edge Asynchronous Reset

```
module dff(D, clk, rstb, Q);  
    input D, clk, rstb;  
    output Q;  
    reg Q;  
    always @(negedge rstb or posedge clk)  
        if (!rstb) begin  
            Q = 0;  
        end  
        else begin  
            Q = D;  
        end  
end  
endmodule
```





# Always for Sequential Logic

- Use “if...else” for conditional logic

```
module my_counter();  
    reg [3:0] counter;  
    wire clk, rstb, enable, up_en, down_en;  
    always @ (posedge clk or negedge rstb)  
        if (rstb == 1' b0) begin  
            counter = 4' b0000;  
  
        end  
        else if (enable == 1' b1 && up_en == 1' b1) begin  
            counter = counter + 1' b1;  
  
        end  
        else if (enable == 1' b1 && down_en == 1' b1) begin  
            counter = counter - 1' b1;  
  
        end  
        else begin  
            counter = counter;  
  
        end  
  
endmodule
```





# For Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
for ( i = 0 ; i <= 15 ; i = i + 1 ) begin
```

```
    output = i;
```

```
    #10;
```

```
end
```



# While Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
i = 0;
```

```
while (i <= 15) begin
```

```
    output = i;
```


```
    #10 i = i + 1;
```

```
end
```


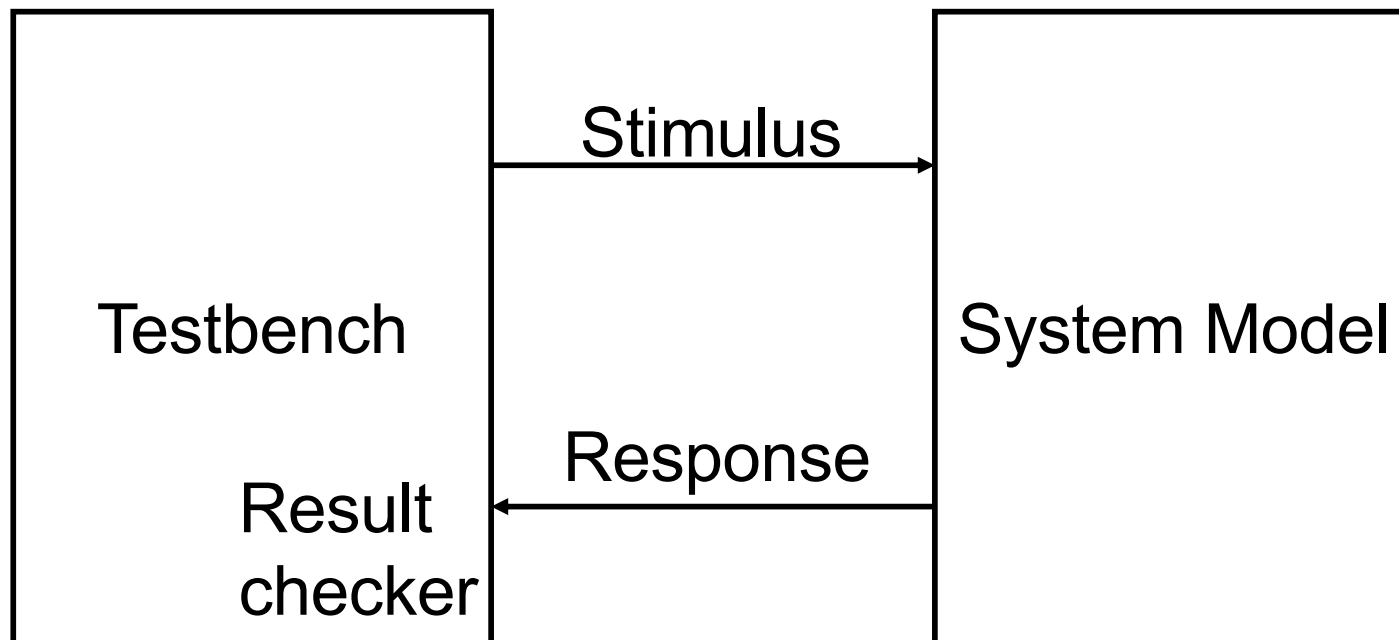
# Simulating Verilog Code

- Testbench: a Verilog module to provide stimuli
- Instantiate circuits under test in testbench
- Pair of stimuli generator and circuit under test run simultaneously





# Writing Testbenches

```
module test;  
reg a, b, sel;
```

← Inputs to device under test

```
mux m(y, a, b, sel);
```

← Device under test

**\$monitor** is a built-in event  
driven “printf” function

```
initial begin
```

```
$monitor($time,, “a = %b b=%b sel=%b y=%b”,  
          a, b, sel, y);
```

```
a = 0; b = 0; sel = 0;
```

```
#10 a = 1;
```

```
#10 sel = 1;
```

```
#10 b = 1;
```

```
end
```

← Stimulus generated by  
sequence of assignments  
and delays

```
end module
```



# More than modeling hardware

- \$monitor — give it a list of variables. When one of them changes, it prints the information. Can only have one of these active at a time.

e.g. ...

- \$monitor (\$time,,, “a=%b, b=%b, sum=%b, cOut=%b”,a, b, sum, cOut);

extra commas to  
print spaces

%b is binary (also, %h,  
%d and others)

- The above will print:

2 a=0, b=0, sum=0, cOut=0<return>

newline  
automatically  
included

- \$display() — sort of like printf()

- \$display (“Hello, world — %h”, hexvalue)

display contents of data item called  
“hexvalue” using hex digits (0-9,A-F)



# Testbench Stimulus



```
module circuit_under_test (A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    wire e;  
    and # (30) g1(e,A,B);  
    or # (20) g3(x,e,y);  
    not # (10) g2(y,C);  
endmodule
```

Specify time delay of circuit  
(not synthesizable, only  
meaningful for the simulator)

```
`timescale 1ns / 100ps  
module stim_crct;  
    reg A,B,C;  
    wire x,y;  
    circuit_under_test c1(A,B,C,x,y);  
    initial  
        begin  
            A = 1'b0; B = 1'b0; C = 1'b0;  
            #100  
            A = 1'b1; B = 1'b1; C = 1'b1;  
            #100 $finish;  
        end  
endmodule
```



# Testbench Stimulus

 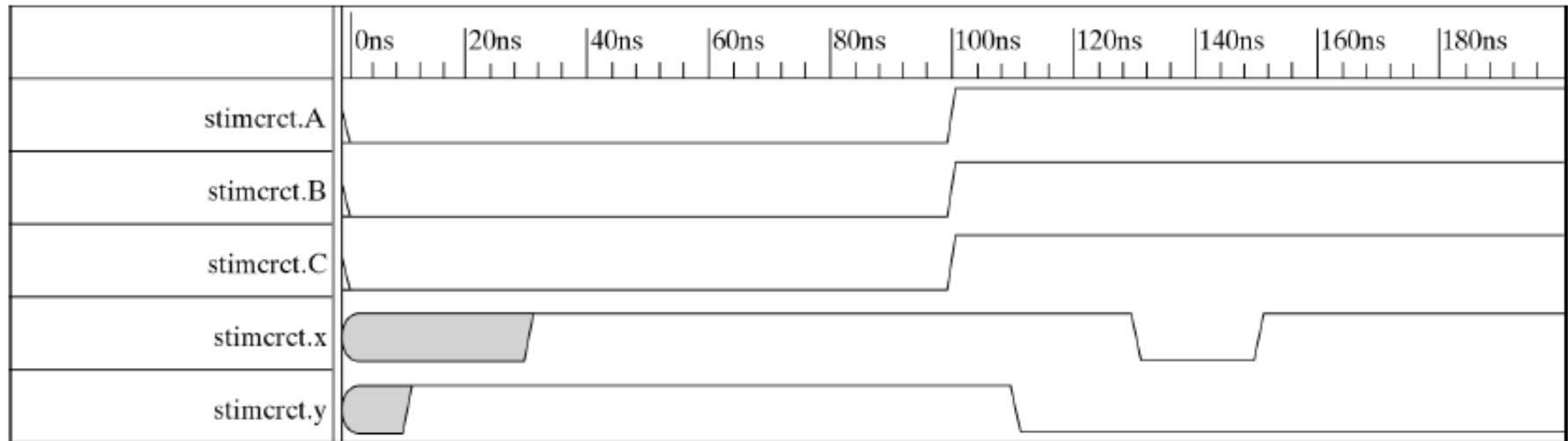



# Discrete-event Simulation

- Basic idea: simulator is active only when it needs to react upon an event (when something changes)
- Main data structure used by simulators
  - Event Queue
  - Contains events labeled with the time stamp at which they are to be executed
- Basic simulation paradigm
  - Execute every event in the queue for the current simulated time
  - These events may change system state and may trigger to schedule new events in the future
  - When there are no events left at the current time instance, advance simulated time to the soonest time stamp of event in the queue





# Simulation Behavior

- Non-preemptive, no priorities
- A process must explicitly request a context switch
- Events at a particular time stamp are unordered



# Two Types of Events

- Evaluation events compute functions of inputs
  - Right hand side of assignments
- Update events change outputs
  - Left hand side of assignments, output ports of modules
- Taking into account **#** delays, non-blocking assignments

Update event writes  
new value of **a** and  
schedules any  
evaluation events  
that are sensitive to  
a change on **a**

$$\mathbf{a} \leq \mathbf{b} + \mathbf{c}$$

Evaluation event reads  
values of **b** and **c**, adds  
them, and schedules an  
update event




# Simulation Behavior

- Concurrent processes (initial, always) run until they stop at one of the following
- #18
  - Schedule process to resume 18 time units from current time stamp
- Wait (BooleanStatement)
  - Resume when Statement becomes true
- @(a, b, y)
  - Resume when a, b, or y changes
- @(posedge clk)
  - Resume when clk changes from 0 to 1



# Example: Adder


## Full Adder:

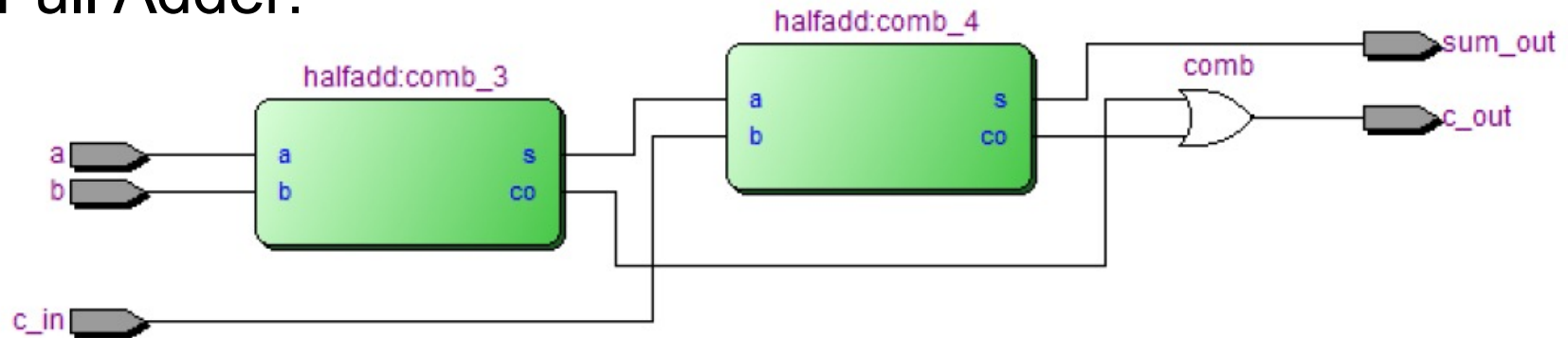


## Half Adder:

Inputs		Outputs	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Truth table

 

Schematic

 

Realization



# Example: Adder

```
// Half Adder
//
module halfadd (a, b,
s, co);
    input a, b;
    output s, co;

    assign s = a ^ b;
    assign co = a & b;
endmodule
```

```
// Full Adder from Half Adders
//
module fulladd (a, b, c_in, sum_out, c_out);
    input a, b, c_in;
    output sum_out, c_out;
    wire s1, c1, c2;

    halfadd ha1(a, b, s1, c1);
    halfadd ha2(s1, c_in, sum_out, c2);

    assign c_out = c1 | c2;
endmodule
```



# Putting it all together

- Computation encapsulated inside a **module**
  - Within a module computation can be described by three methods
    - Components instances - Structural
    - Direct/concurrent assignments - RTL
    - Procedures
      - **initial**: only used for simulation purposes in testbench codes
      - **always**: can be used to describe any behavior



# Putting it all together

- Computation encapsulated inside a **module**
  - Within a module computation can be described by three methods
    - 1 Components instances - Structural
    - 2 Direct/concurrent assignments - RTL
    - 3 Procedures
      - **initial**: only used for simulation purposes in testbench codes
      - **always**: can be used to describe any behavior



# 1. Structural: Using component instances

```
// Full Adder from Half Adders and Additional Logic Pieces
//
module fulladd (a, b, c_in, sum_out, c_out);
    input a, b, c_in;
    output sum_out, c_out;
    wire s1, c1, c2;


    halfadd ha1(a, b, s1, c1);
    halfadd ha2(s1, c_in, sum_out, c2);
    carryout_block co1 (c1, c2, c_out);

endmodule
```





# How do you create a project like that?

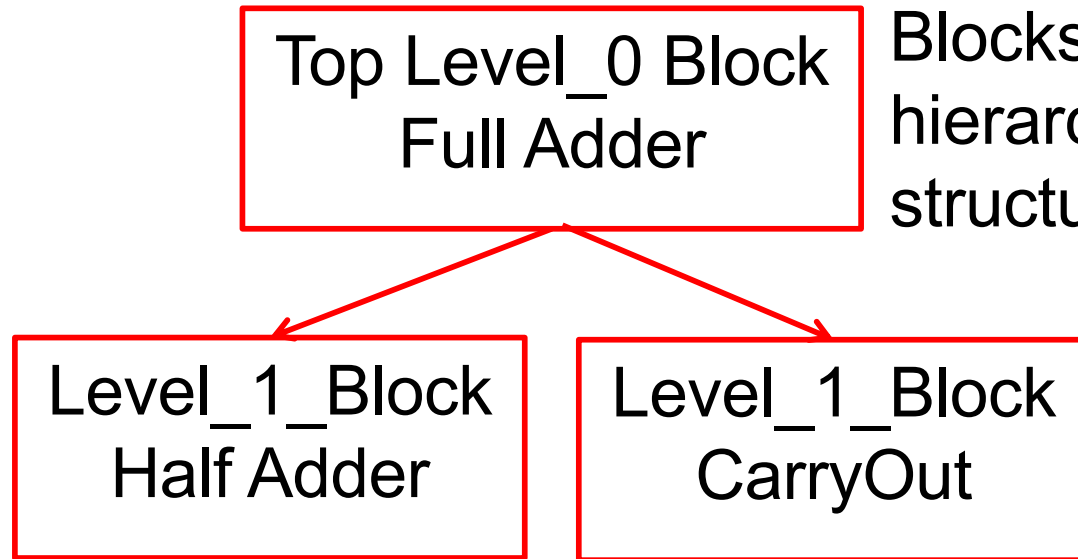


Blocks at the very top of hierarchy are described structurally

Need to describe the function of Half Adder:  
All blocks at the bottom of the hierarchy must have a behavioral or RTL description

Need to describe the function of CarryOut:  
All blocks at the bottom of the hierarchy must have a behavioral or RTL description



# How do you create a project like that?

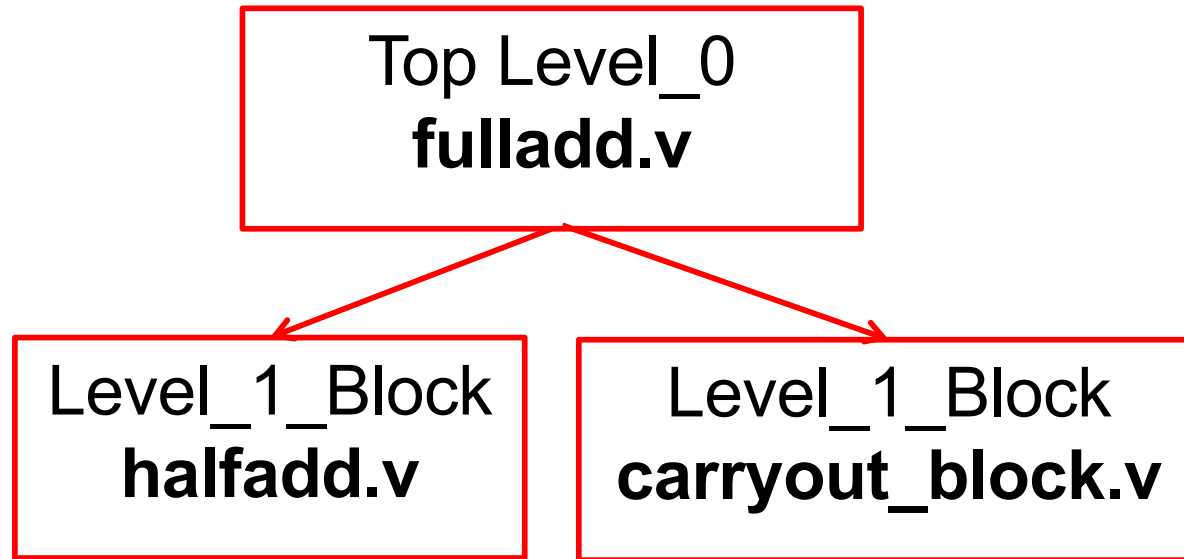

Can be composed of three verilog files:

carryout\_block.v, halfadd.v, fulladd.v

In addition, each design file can have its dedicated testbench verilog file for its simulation



## 2. RTL Description Halfadd.v

```
// Half Adder
//
module halfadd (a, b,
s, co);
    input a, b;
    output s, co;

    assign s = a ^ b;
    assign co = a & b;
endmodule
```



# RTL Description Carryout\_block.v

```
// CarryOut
//
Module carryout_block (c1, c2, co);
    input c1, c2;
    output co;

    assign co = c1 & c2;
endmodule
```



# Fulladd.v

```
// Full Adder from Half Adders
//
module fulladd (a, b, c_in, sum_out, c_out);
    input a, b, c_in;
    output sum_out, c_out;
    wire s1, c1, c2;

    halfadd ha1(a, b, s1, c1);
    halfadd ha2(s1, c_in, sum_out, c2);

    carryout_block cout1 (c1, c2, c_out);

endmodule
```



# Putting it all together

- Computation encapsulated inside a **module**
  - Within a module computation can be described by three methods
    - 1 Components instances - Structural
    - 2 Direct/concurrent assignments - RTL
    - 3 Procedures
      - **initial**: only used for simulation purposes in testbench codes
      - **always**: can be used to describe any behavior



# Halfadd.v

```
// Half Adder
//
module halfadd (a, b, s, co);
    input a, b;
    output s, co;

    assign s = a ^ b;
    assign co = a & b;
endmodule
```

This style was used to describe the half adder in RTL style:

Signature statement is **assign**

Boolean or arithmetic operators directly applied on signal values on the right hand side



# Putting it all together

- Computation encapsulated inside a **module**
  - Within a module computation can be described by three methods
    - 1 Components instances - Structural
    - 2 Direct/concurrent assignments - RTL
    - 3 Procedures
  - **initial**: only used for simulation purposes in testbench codes
  - **always @**: can be used to describe any behavior






# Always procedure

- You can package statements of both RTL and Behavioral Style inside the `always@` procedure
  - RTL, as a sequence of concurrent assignments
    - corresponding to combinational logic
    - Boolean or arithmetic operators on the right hand side of assignments
  - Behavioral, sequential statements
    - Corresponding to combinational or sequential logic
    - if-else statement


 
# Always procedure with RTL statements


```
module pure_gate (I1, I2, g_out);  
  input I1, I2;  
  output g_out;  
  
  always @(I1, I2) begin  
    g_out <= I1 OR I2;  
  end;  
end module;
```




 
# Always procedure with behavioral statements

```
Module seq_logic (I1, I2, clk, g_out);  
  input I1, I2, clk;  
  output g_out;  
  
  always @(posedge clk) begin  
    g_out <= I1 OR I2;  
  end;  
end module;
```





# Simulation Environment

- Build a Verilog testbench
- Use simulator to simulate waveforms



# Simulation Environment

- Simulation RTL vs Gate Netlist
  - Ideally both should give the same results
  - RTL
    - Only the high level behavior of your design
    - No delay from transition
    - No gate level implementation and signals
  - Gate netlist (synthesized from RTL)
    - Show delay from gates
    - May be different from RTL if synthesis has issue
    - Should be run to verify correctness of RTL