

# Lecture 10

## Finite State Machine

---




# Outline

- Basics of Finite State Machine (\*\*\*)
- State Reduction (\*\*\*)
- Textbook chapters: 9.1-9.4


 
# Finite State Machines

- A mathematical representation which can describe sequential logic circuits
- Computation can be considered as a sequence of steps, each step is a state, and the computation is a sequence of steps (states) which the circuit executes (visits)
- At any given point in time we can freeze the execution and associate the 'state' of the circuit with the content of the memory elements
  - $[A, B, C, D, X, Y]$  can be thought of as a binary code (of 6 bits) that uniquely identifies a state
  - This circuit can possibly exhibit one of  $2^6$  states, i.e., a finite number of states can be encoded





# Building Finite State Machines

- We will first review an example



# Example: Sequence Detector

**Assert output whenever a sequence of [1 0] is detected in the input stream  
Otherwise output is 0**

**Input 1 0 0 1 1 0 1 0 1 1 1 0**

**Output 0 1 0 0 0 1 0 1 0 0 0 1**




# Process for creating a circuit for FSM

- 1. Analyze the verbal problem statement*
- 2. Create example input/output sequences that represent typical scenarios*
- 3. Going through these sequences,*
  - a. Either create a new state and branch out for the corresponding input case*
  - b. Revisit an existing state that covers this input behavior*
- 4. For each state, transitions for all possible input combinations must be accounted for*
- 5. For each possible transition, the output response must be attached*


 
# Process for creating a circuit for FSM


- Always start with the 'initial'/'reset' state
  - How will the circuit react for all input cases starting at this state?




 
# Process for creating a circuit for FSM

- How will the circuit react for all input cases starting at this state
  - If input is '0' that will be the case of the FSM 'having spotted a 0': a new state S2
  - If input is '1' that will be the case of the FSM having spotted a 1': different that spotting a '0', a new state S3
  - In both of these new states output is still '0' no '10' pattern detected







 
# Process for creating a circuit for FSM


- Cover all outgoing transitions from each new state added
  - @S2:
    - If input is '0' the status of the FSM is no different, self loop back to S2
    - If input is '1' that is the first '1' spotted yet, which is the same situation as being in S3, transition to S3
  - @S3:
    - If input is '0' that is a '10' pattern DETECTED, this is a new event, NEW State S4, with output of new state = '1'
    - If input is '1' the status of the FSM is no different, self loop back to S3




 
# Process for creating a circuit for FSM

- Cover all outgoing transitions from each new state added
  - @S4:
    - If input is '0', this is no different than having seen 'just any sequence' 0s, transition to S2
    - If input is '1', this is no different than having seen 'just any sequence' 1s, transition to S3





# Finite State Machine Basics

- State updated at rising edge of clock
- With  $n$  bits, we can realize  $2^n$  states in total
- Two types of FSM: Mealy or Moore State Machine

Mealy Machine:

Next state =  $F(\text{current state}, \text{input})$

Output =  $G(\text{current state}, \text{input})$


Moore Machine:

Next state =  $F(\text{current state}, \text{input})$

Output =  $G(\text{current state})$




# Moore versus Mealy machines

 
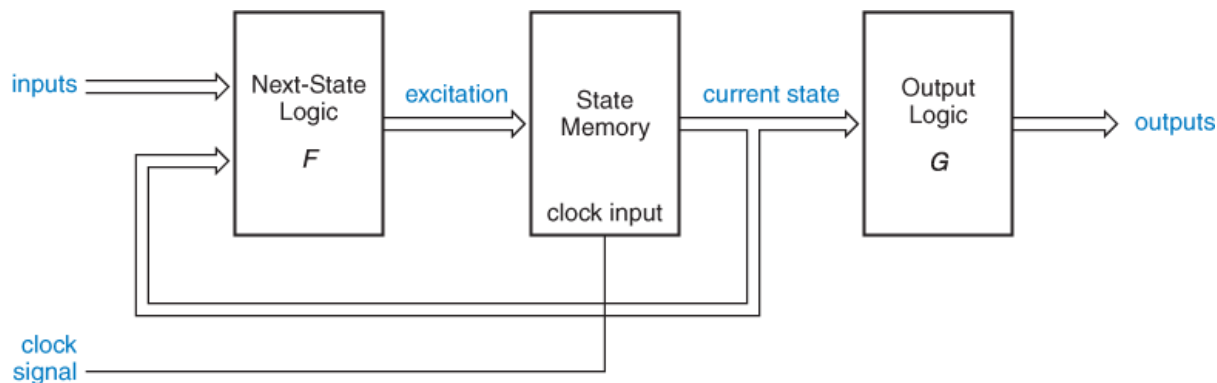
## Mealy machine

Outputs depend on state  
and on inputs

Input changes can cause  
immediate output changes  
**(asynchronous)**




## Moore machine

Outputs are a function  
of current state

Outputs change  
synchronously with  
state changes



# Timing Diagram of FSM

 

- Note that the outputs of Moore's machine are synchronous while Mealy's are not




# Comparing Moore and Mealy machines

- Mealy state machines
  - + Typically have fewer states
  - + React faster to inputs — don't wait for clock
  - Asynchronous outputs can be dangerous
- Moore state machines
  - + Safer to use because outputs change at clock edge
  - May take additional logic to decode state into outputs
- Alternatively, design synchronous Mealy machines
  - Design a Mealy machine
  - Then register the outputs


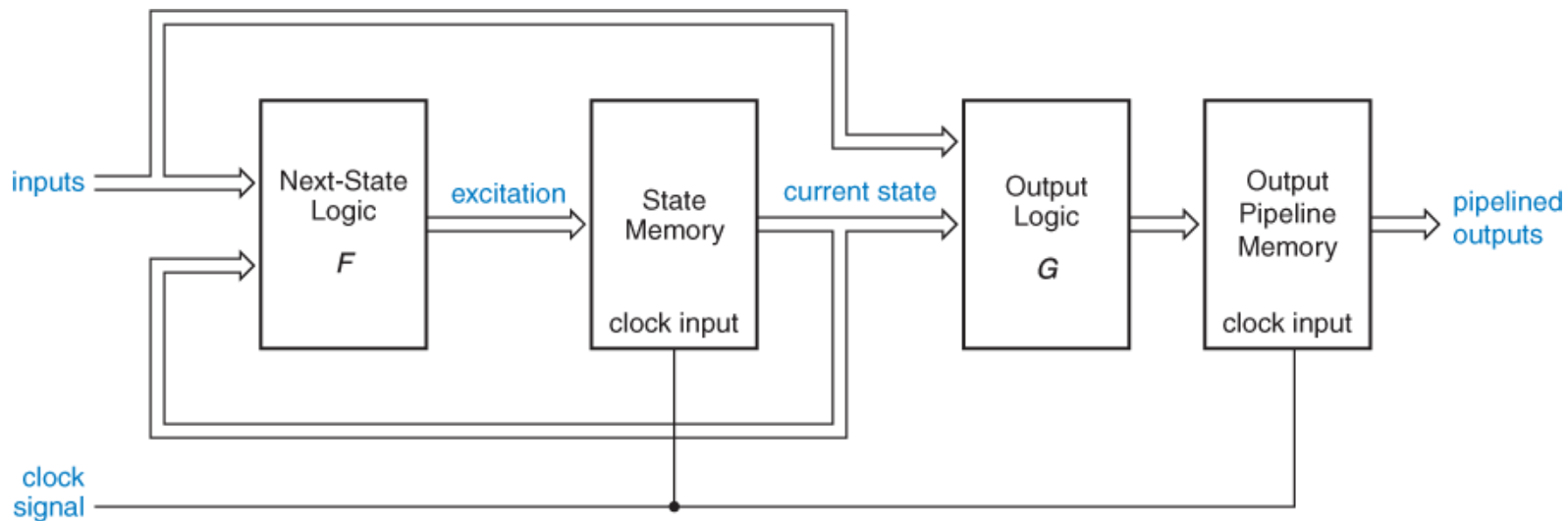
# Mealy Machine with Pipelined Outputs


- Registered state **and registered outputs**
  - No glitches on outputs
  - No race conditions between communicating machines






# State Diagram

MAX/MAXS is output

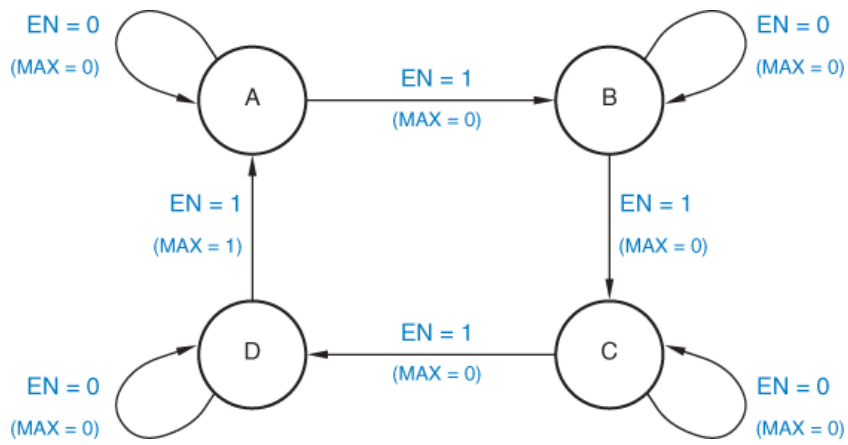

Mealy Machine

 

Moore Machine

- Use graphical format to represent state transition table





# FSM Example

Transition Table

Q1Q0	Q1*Q0*	
Q1Q0	EN=0	EN=1
00	00	01
01	01	10
10	10	11
11	11	00

State Table

S	S*	
	EN=0	EN=1
A	A	B
B	B	C
C	C	D
D	D	A


State/Output Table

S	S*, MAX	
	EN=0	EN=1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1

- Use tables to represent transition relationships
- Can use alphanumeric state names , e.g. A, B, S0, S1 to replace "00", "01" etc.



# FSM Example

 

$$D0 = Q0 \cdot EN' + Q0' \cdot EN$$

$$D1 = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

$$Q0^* = D0$$

$$Q1^* = D1$$



**transition equation**

$$Q0^* = Q0 \cdot EN' + Q0' \cdot EN$$

$$Q1^* = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

**output equation**

$$MAX = Q1 \cdot Q0 \cdot EN$$

- Circuits are built to realize transition table/equations




# State Minimization

Implement FSM with fewest possible states

- Least number of flip-flops  
Number of distinct states to be encoded correlates with the number of flip flops that will store the codes for those states
- Boundaries are power of two number of states
- Reduce the number of gates needed for implementation of the combinational logic that fires up the state code contents of the memory elements




# State Reduction

 

	Next state		
Present State	I = 0	I = 1	Output
A	A	B	0
B	C	B	0
C	A	B	0
D	A	A	1



# State Reduction

 


**Same next state  
for same input  
AND same output**

	Next state		
Present State	I = 0	I = 1	Output
A	A	B	0
B	C	B	0
C	A	B	0
D	A	A	1



# State Reduction

 

	Next state		
Present State	I = 0	I = 1	Output
AC	AC	B	0
B	AC	B	0
D	AC	AC	1


**A and C are equivalent**

**Give a common new name (AC) and let one of them also represent both (remove one state from the table)**

**Update all states named A or C as AC**



# State Reduction

 

	Next state		
Present State	I = 0	I = 1	Output
ABC	ABC	ABC	0
D	ABC	ABC	1

**AC and B are equivalent**

**Give a common new name (ABC) and let one of them also represent both (remove one state from the table)**

**Update all states named AC or B as ABC**



# State Reduction

Identify and combine states that have equivalent behavior

*Equivalent States:* for all input combinations, states transition to the same or equivalent states, as well as same output behavior





# State Reduction

## *Algorithmic Approach!!!*

- Start with state transition table
- Identify states with same output behavior
- If such states transition to the same next state, they are equivalent
- Combine into a single new renamed state
- Repeat until no new states are combined

*But How??*



# Systematic Approach to State Reduction

- Sometimes equivalency is not so obvious
- Implication Chart



# Implication Chart

Current state	Next state		output
	I=0	I=1	
A	B	E	0
B	C	D	0
C	D	D	0
D	A	A	1
E	D	D	0

It is not obvious whether A and B are equivalent

If A and B were to be equivalent, then

B and C have to be equivalent

E and D have to be equivalent

In this case, we see that E and D are not (their output behavior does not match), hence this implies that A and B cannot be equivalent



# Implication Chart

1. Construct implication chart, one square for each combination of states taken two at a time


B				
C				
D				
E				
	A	B	C	D



# Implication Chart

1. Construct implication chart, one square for each combination of states taken two at a time
2. Square labeled  $(S_i, S_j)$ 
  - if outputs differ than square gets  $X$
  - Otherwise write down implied state pairs for all input combinations
  - If the equivalency is directly observable the square gets 1

B	B=C D=E			
C	B=D D=E	C=D		
D	X	X	X	
E	B=D D=E	C=D	1	X
	A	B	C	D

 

	Next state		
Current state	I=0	I=1	output
A	B	E	0
B	C	D	0
C	D	D	0
D	A	A	1
E	D	D	0



# Implication Chart

2. Square labeled ( $S_i, S_j$ )
  - if outputs differ then square gets  $X$
  - Otherwise write down implied state pairs for all input combinations
  - If the equivalency is directly observable the square gets 1
3. Advance through chart top-to-bottom and left-to-right
  - If square ( $S_i, S_j$ ) contains next state pair  $S_m, S_n$  and that pair has a square already labeled  $X$ , then  $S_i, S_j$  is also labeled  $X$

B	B=C D=E			
C	B=D D=E	C=D		
D	X	X	X	
E	B=D D=E	C=D	1	X
	A	B	C	D




B	X			
C	X	C=D		
D	X	X	X	
E	X	C=D	1	X
	A	B	C	D



# Implication Chart

 2. Square labeled ( $S_i, S_j$ )
  - if outputs differ than square gets  $X$
  - Otherwise write down implied state pairs for all input combinations
  - If the equivalency is directly observable the square gets 1
3. Advance through chart top-to-bottom and left-to-right
  - If square ( $S_i, S_j$ ) contains next state pair  $S_m, S_n$  and that pair has a square already labeled  $X$ , then  $S_i, S_j$  is also labeled  $X$





# Implication Chart

2. Square labeled ( $S_i, S_j$ )
  - if outputs differ than square gets  $X$
  - Otherwise write down implied state pairs for all input combinations
  - If the equivalency is directly observable the square gets 1
3. Advance through chart top-to-bottom and left-to-right
  - If square ( $S_i, S_j$ ) contains next state pair  $S_m, S_n$  and that pair has a square already labeled  $X$ , then  $S_i, S_j$  is also labeled  $X$
4. Continue executing Step 3 until no new squares are marked with  $X$
5. For each remaining unmarked square  $S_i, S_j$ , then conclude  $S_i$  and  $S_j$  are equivalent

B	X			
C	X	X		
D	X	X	X	
E	X	X	1	X
	A	B	C	D

C and E are the only equivalent pair






# Implication Chart-Summary

1. Construct implication chart, one square for each combination of states taken two at a time
2. Square labeled  $(S_i, S_j)$ 
  - if outputs differ than square gets  $X$
  - Otherwise write down implied state pairs for all input combinations
3. Advance through chart top-to-bottom and left-to-right
  - If square  $(S_i, S_j)$  contains next state pair  $S_m, S_n$  and that pair has a square already labeled  $X$ , then  $S_i, S_j$  is also labeled  $X$
4. Continue executing Step 3 until no new squares are marked with  $X$
5. For each remaining unmarked square  $S_i, S_j$ , then conclude  $S_i$  and  $S_j$  are equivalent



# Multiple Input State Diagram Example

 


**State Diagram**

Present State	Next State				Output
	00	01	10	11	
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	1
S <sub>1</sub>	S <sub>0</sub>	S <sub>3</sub>	S <sub>1</sub>	S <sub>5</sub>	0
S <sub>2</sub>	S <sub>1</sub>	S <sub>3</sub>	S <sub>2</sub>	S <sub>4</sub>	1
S <sub>3</sub>	S <sub>1</sub>	S <sub>0</sub>	S <sub>4</sub>	S <sub>5</sub>	0
S <sub>4</sub>	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>5</sub>	1
S <sub>5</sub>	S <sub>1</sub>	S <sub>4</sub>	S <sub>0</sub>	S <sub>5</sub>	0

**Symbolic State Diagram**



# Example (contd)

 

Present State	Next State				Output
	00	01	10	11	
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	1
S <sub>1</sub>	S <sub>0</sub>	S <sub>3</sub>	S <sub>1</sub>	S <sub>5</sub>	0
S <sub>2</sub>	S <sub>1</sub>	S <sub>3</sub>	S <sub>2</sub>	S <sub>4</sub>	1
S <sub>3</sub>	S <sub>1</sub>	S <sub>0</sub>	S <sub>4</sub>	S <sub>5</sub>	0
S <sub>4</sub>	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>5</sub>	1
S <sub>5</sub>	S <sub>1</sub>	S <sub>4</sub>	S <sub>0</sub>	S <sub>5</sub>	0

Minimized State Table

**S3 and S5  
S0 and S4  
are equivalent**



# Appendix