

HW#2 Tianpu Zhao

#1 (1) $f(a,b,c,d) = S(0,5,6,10,11,13) + d(4,8,14)$


Implication table:

decimal	binary	
S {	0	0000
	5	0101
	6	0110
	10	1010
	11	1011
	13	1101
d {	4	0100
	8	1000
	14	1110

group by # of 1's →

0000
0100
1000
0101
0110
1010
1011
1101
1110

Find prime implicants:

 

Find unate covering:

Minterms / Prime implicants	0x00	X000	010x	01x0	10x0	x101	x110	101x	1x10
0000	1	1							
0100	1		1	1					
1000		1			1				
0101			1			1			
0110				1			1		
1010					1			1	1
1011								1	
1101						1			
1110							1		1

○ : essential prime implicants & corresponding minterms

↓ eliminate essential prime implicants & corresponding rows

Minterms / Prime implicants	0x00	X000	010x	01x0	10x0	x110	1x10
0000	1	1					
0100	1		1	1			
1000		1			1		
0110				1		1	
1110						1	1

01X0 column dominates 010X, X000 column dominates 10X0,
 X110 column dominates 1X10, eliminate dominated columns:

Minterms Prime implicants	0X00	X000	01X0	X110
0000	1	1		
0100	1		1	
1000		1		
0110			1	1
1110				1

0110 dominates 1110, 0000 dominates 1000, eliminate

0110, 0000

Minterms Prime implicants	0X00	X000	01X0	X110
0100	1		1	
1000		1		
1110				1

$X110$, $X000$ are essential prime implicants; either $0X00$ or $01X0$ can fulfill 0100 . Thus the simplified expression is:

$$f(a,b,c,d) = a'c'd' + b'c'd' + bcd' + bc'd + ab'c$$


Note: 0100 is a don't care minterm. So there is no need for including $a'c'd'$. In fact, following KMap the simplest expression includes exactly the rest 4 terms.

$$(2) f(a,b,c) = \sum(0, 2, 3, 4, 5, 7)$$

decimal	binary	
0	000 .	000
2	010 .	010
3	011 .	100
4	100 .	011
5	101 .	101
7	111	111

→
group

prime implicants:

 

prime implicants Minterms	0x0	x00	01x	10x	x11	1x1
000	1	1				
010	1		1			
100		1		1		
011			1		1	
101				1		1
111					1	1

Unate covering: no dominant, perform branch & bound.

Disjoint rows = 3 (pick 111, 100, 010, for example)
 \Rightarrow the lower bound $L=3$.

Pick one path for round (1):

* pick 0x0, erase rows 000, 010

prime minterms	x_0x_1	x_1x_2	x_0x_2	x_1x_3	x_0x_3
100	1		1		
011		1		1	
101			1		1
111				1	1

x_0x_2 dominates x_0x_1 , erase x_0x_1 , x_1x_3 dominates x_0x_3 ,
 erase x_0x_3

prime minterms	x_0x_2	x_1x_3	x_0x_3
100	1		
011		1	
101	1		1
111		1	1

101 dominates 100, remove 101, 111 dominates 011, remove 111

Prime minterms	10X	X11
100	1	
011		1

Left 10X and X11 as prime implicants. together with 0X0 forms the expression. The solution matches the lower bound thus is an optimal solution.

$$f(a,b,c) = a'c' + ab' + bc.$$

#2

Signed = S
unsigned = U

Decimal = D
Binary = B
Octal = O
Hex = H

	Signed Or Unsigned	Width	Base: Decimal, Binary, Octal, Hexadecimal, etc.	Equivalent Integer Value
8'b00001000	U	8	B	8
16'hABCD	U	16	H	43981
4'sb1110	S	4	B	-2
4'd12	U	4	D	12
4'b1100	U	4	B	12
8'shFF	S	8	H	-1
8'sb00011100	S	8	B	28
12'h2A8	U	12	H	680
6'sb111101	S	6	B	-3
12'o3456	U	12	O	1838

#3

Codes:

```
// Q3_dec_2_to_4_output_pol_ctrl.v
`timescale 1ns/1ps
module dec_2_to_4_output_pol_ctrl (
    input A0, A1, A2,
    output Y0, Y1, Y2, Y3
);
    // inverters and the and gates
    wire d0, d1, d2, d3;
    assign d0 = (~A1 & ~A0);
    assign d1 = (~A1 & A0);
    assign d2 = (A1 & ~A0);
    assign d3 = (A1 & A0);

    // xors
    assign Y0 = d0 ^ A2;
    assign Y1 = d1 ^ A2;
    assign Y2 = d2 ^ A2;
    assign Y3 = d3 ^ A2;
endmodule
```

Testbench:

```
// Q3_tb_dec_2_to_4.v
`timescale 1ns/1ps

module tb;
    // DUT input signals
    reg A0, A1, A2;
    // DUT output signals
    wire Y0, Y1, Y2, Y3;
    // index for loop
    integer i;

    // DUT
    dec_2_to_4_output_pol_ctrl dut (
        .A0(A0), .A1(A1), .A2(A2),
        .Y0(Y0), .Y1(Y1), .Y2(Y2), .Y3(Y3)
    );

    // print table
    initial begin
        $display("A2 A1 A0 | Y3 Y2 Y1 Y0");
        $display("-----");

        // create all combinations for the input
        for (i = 0; i < 8; i = i + 1)
            begin
                {A2, A1, A0} = i[2:0];
                #1; // wait 1ns
                $display(" %b %b %b | %b %b %b %b",
                    A2, A1, A0, Y3, Y2, Y1, Y0);
            end
        $display("-----");
        $finish;
    end
endmodule
```

Output

```
xcelium>
xcelium> source /vol/cadence2018/XCELIUM1809/tools/xcelium/files/xmsimrc
xcelium> run
A2 A1 A0 | Y3 Y2 Y1 Y0
-----
0 0 0 | 0 0 0 1
0 0 1 | 0 0 1 0
0 1 0 | 0 1 0 0
0 1 1 | 1 0 0 0
1 0 0 | 1 1 1 0
1 0 1 | 1 1 0 1
1 1 0 | 1 0 1 1
1 1 1 | 0 1 1 1
-----
Simulation complete via $finish(1) at time 8 NS + 0
./q3_tb_dec_2_to_4.v:31 $finish;
xcelium> |
```

#4

Codes:

// Q4_full_adder.v

```
`timescale 1ns/1ps
module full_adder (
    input A,
    input B,
    input CIN,
    output S,
    output COUT
);
    assign S = A ^ B ^ CIN;
    assign COUT = (A & B) | (A & CIN) | (B & CIN);
endmodule
```

```
module ripple_adder4 (
    input [3:0] A,
    input [3:0] B,
    input CIN,
    output [3:0] S,
    output COUT
);
    wire C1, C2, C3;

    assign S[0] = A[0] ^ B[0] ^ CIN;
    assign C1 = (A[0] & B[0]) | (A[0] & CIN) | (B[0] & CIN);
    assign S[1] = A[1] ^ B[1] ^ C1;
    assign C2 = (A[1] & B[1]) | (A[1] & C1) | (B[1] & C1);
    assign S[2] = A[2] ^ B[2] ^ C2;
    assign C3 = (A[2] & B[2]) | (A[2] & C2) | (B[2] & C2);
    assign S[3] = A[3] ^ B[3] ^ C3;
    assign COUT = C3;
```

Testbench

```
// Q4_tb_full_adder.v
```

```
`timescale 1ns/1ps
module tb_ripple_adder4;
    reg [3:0] A, B;
    reg CIN;
    wire [3:0] S;
    wire COUT;

    ripple_adder4 dut (.A(A), .B(B), .CIN(CIN), .S(S), .COUT(COUT));

    task run_vec;
        input [3:0] a, b, cin;
        begin
            A = a; B = b; CIN = cin;
            #1;
            $display("A=%0d (%b) B=%0d (%b) CIN=%0d -> COUT=%0b, S=%04b, {COUT, S}=%0d",
                a, a, b, b, cin, COUT, S, {COUT, S});
        end
    endtask

    initial begin
        $display("---- 4-bit Ripple Carry Adder Test ----");

        // initialize
        A=0; B=0; CIN=0;
        #1;

        run_vec(4'd1 , 4'd3 , 1'b0);
        run_vec(4'd11, 4'd9 , 1'b0);
        run_vec(4'd7 , 4'd13, 1'b0);
        run_vec(4'd15, 4'd1 , 1'b0);

        $display("All tests completed.");
        $finish;
    end
endmodule
```

Output

```
xcelium>
xcelium> source /vol/cadence2018/XCELIUM1809/tools/xcelium/files/xmsimrc
xcelium> run
---- 4-bit Ripple Carry Adder Test ----
A=1 (0001)  B=3 (0011)  CIN=0 -> COUT=0, S=0100, {COUT, S}=4
A=11 (1011) B=9 (1001)  CIN=0 -> COUT=1, S=0100, {COUT, S}=20
A=7 (0111)  B=13 (1101) CIN=0 -> COUT=1, S=0100, {COUT, S}=20
A=15 (1111) B=1 (0001)  CIN=0 -> COUT=1, S=0000, {COUT, S}=16
All tests completed.
Simulation complete via $finish(1) at time 5 NS + 0
./q4_tb_full_adder.v:33      $finish;
xcelium> |
```